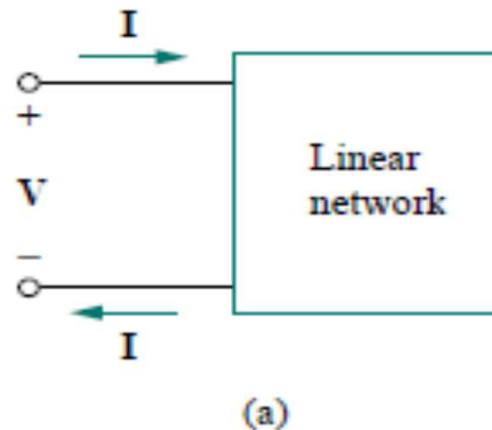


TWO-PORT CIRCUITS




INTRODUCTION

- A pair of terminals through which a current may enter or leave a network is known as a *port*.
- Two-terminal devices or elements (such as resistors, capacitors, and inductors) result in *one-port networks*.
- Most of the circuits we have dealt with so far are two-terminal or *one-port circuits*, represented in the following figure 1(a):



INTRODUCTION

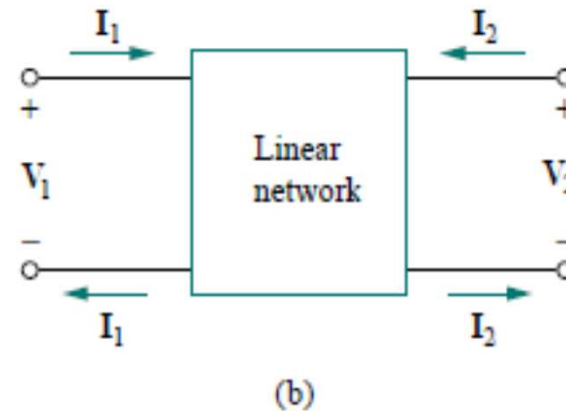- The four-terminal or *two-port circuits* are involving op amps, transistors, and transformers, as shown in the following figure 1(b):



- *A port is an access to the network and consists of a pair of terminals.*
- The current entering one terminal leaves through the other terminal so that the net current entering the port equals zero.




INTRODUCTION

- *A two-port network is an electrical network with two separate ports for input and output.*
- A two-port network has *two terminal pairs* acting as access points.
- Such networks are useful in communications, control systems, power systems, and electronics. *For example, they are used in electronics to model transistors and to apply the analysis of transistor circuits.*
- The current entering one terminal of a pair leaves the other terminal in the pair.



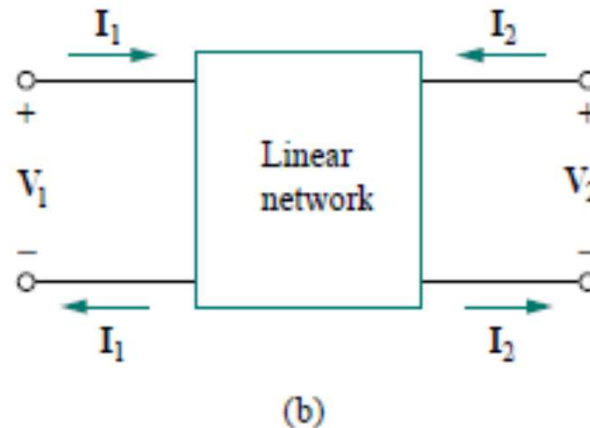To characterize a two-port network requires that we relate the terminal quantities V_1 , V_2 , I_1 , and I_2 in Fig. 1(b).




- The various terms that relate these voltages and currents are called *parameters*.
- Our goal is to derive *six sets* of these parameters.
- We will show the relationship between these parameters and how two-port networks can be connected in series, parallel, or cascade.



IMPEDANCE PARAMETERS

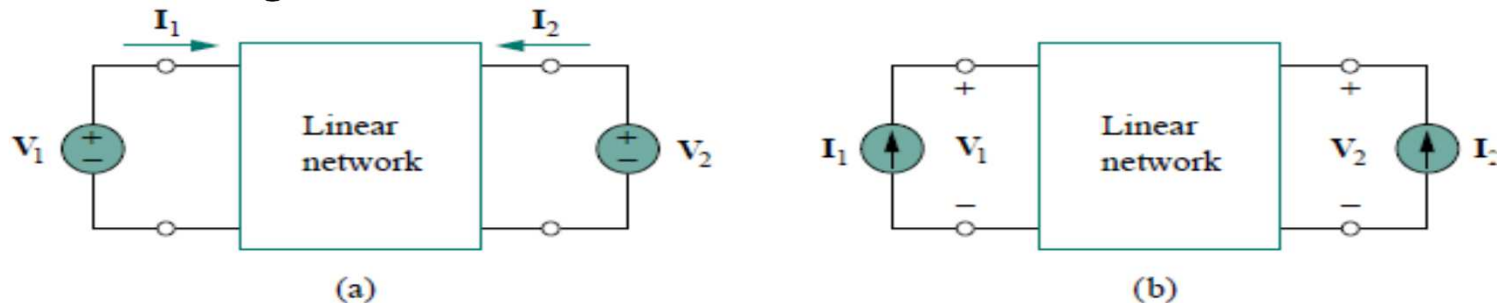- *Impedance and admittance parameters* are commonly used in the synthesis of filters.
- A **two-port network** may be voltage-driven as in Fig. 2(a) or current-driven as in Fig. 2(b).



- The terminal voltages can be related to the terminal currents as:

$$\begin{cases} V_1 = z_{11}I_1 + z_{12}I_2 \\ V_2 = z_{21}I_1 + z_{22}I_2 \end{cases}$$

or in matrix form as

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$



the **Z** terms are called the *z parameters*, and have units of ohms.

- The values of the parameters can be evaluated by setting $I_1 = 0$
- or $I_2 = 0$. Thus,



$$\left[\begin{array}{ll} z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}, & z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \\ z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}, & z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \end{array} \right]$$

- Since the *z parameters* are obtained by open-circuiting the input or output port, they are also called the *open-circuit impedance parameters*.
- z_{11} = Open-circuit input impedance
- z_{12} = Open-circuit transfer impedance from port 1 to port 2
- z_{21} = Open-circuit transfer impedance from port 2 to port 1
- z_{22} = Open-circuit output impedance




We obtain Z_{11} and Z_{21} by connecting a voltage V_1 (or a current source I_1) to port 1 with port 2 open-circuited as in Fig.3(a) and finding I_1 and V_2

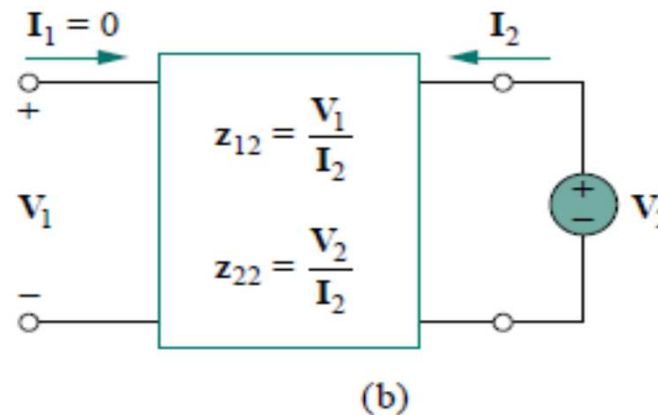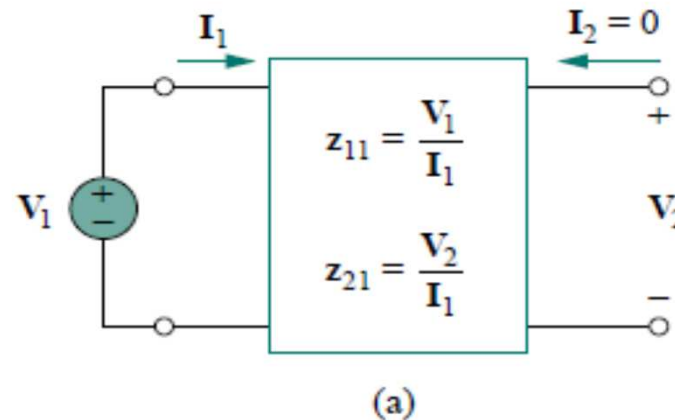- Similarly, we obtain Z_{12} and Z_{22} by connecting a voltage V_2 (or a current source I_2) to port 2 with port 1 open-circuited as in Fig. 3(b) and finding I_2 and V_1




Sometimes \mathbf{Z}_{11} and \mathbf{Z}_{22} are called *driving-point impedances*, while \mathbf{Z}_{21} and \mathbf{Z}_{12} are called *transfer impedances*.

- When $\mathbf{Z}_{11} = \mathbf{Z}_{22}$, the two-port network is said to be *symmetrical*.
- When the two-port network has *no dependent sources*, the transfer impedances are equal ($\mathbf{Z}_{12} = \mathbf{Z}_{21}$), and the two-port is said to be *reciprocal*.
- A two-port is *reciprocal* if *interchanging* an ideal voltage source at one port with an ideal ammeter at the other port gives the same ammeter reading.
- The reciprocal network yields $\mathbf{V} = \mathbf{z}_{12}\mathbf{I}$ when connected as in Fig. 4(a), but yields $\mathbf{V} = \mathbf{z}_{21}\mathbf{I}$ when connected as in Fig. 4(b).

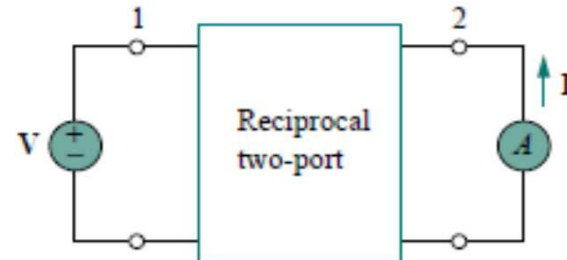

(a)


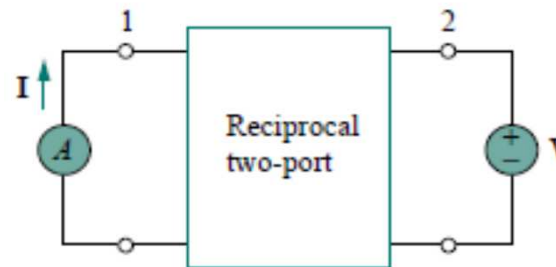


(b)






For a reciprocal network, the T-equivalent circuit in Fig.5(a) can be used.

- If the network is not reciprocal, a more general equivalent network is shown in Fig. 5(b)

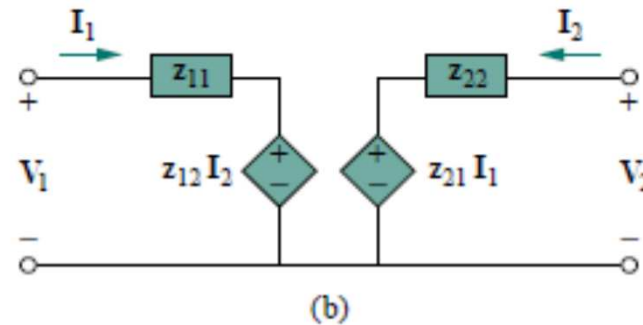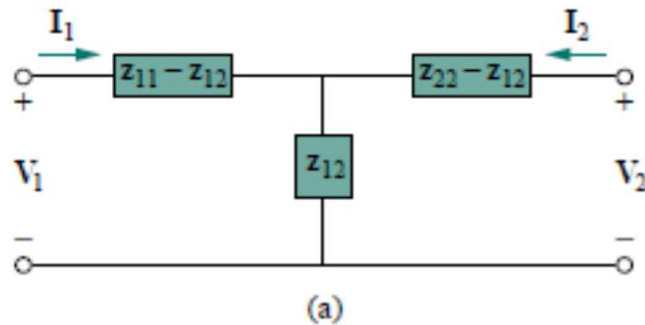

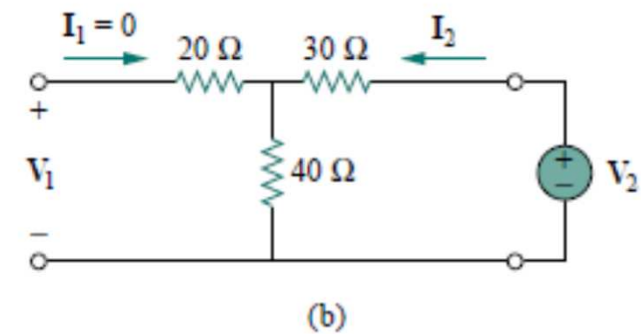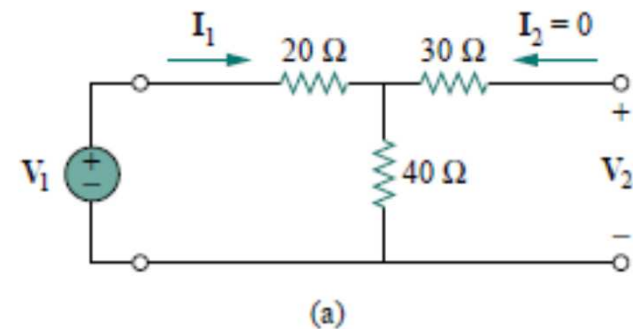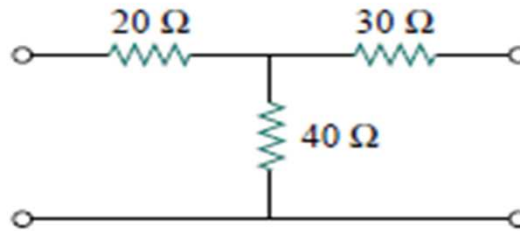Example. 1

- Determine the Z parameters for the circuit in the following figure:



Solution:

To determine z_{11} and z_{21} , we apply a voltage source V_1 to the input port and leave the output port open as in Fig. (a). Then,

$$z_{11} = \frac{V_1}{I_1} = \frac{(20 + 40)I_1}{I_1} = 60 \Omega$$

that is, z_{11} is the input impedance at port 1.



$$z_{21} = \frac{V_2}{I_1} = \frac{40I_1}{I_1} = 40 \Omega$$

To find z_{12} and z_{22} , we apply a voltage source V_2 to the output port and leave the input port open as in Fig (b). Then,

$$z_{12} = \frac{V_1}{I_2} = \frac{40I_2}{I_2} = 40 \Omega, \quad z_{22} = \frac{V_2}{I_2} = \frac{(30 + 40)I_2}{I_2} = 70 \Omega$$

Thus,



$$[z] = \begin{bmatrix} 60 \Omega & 40 \Omega \\ 40 \Omega & 70 \Omega \end{bmatrix}$$

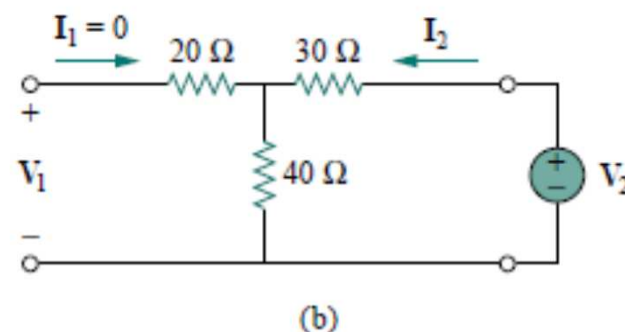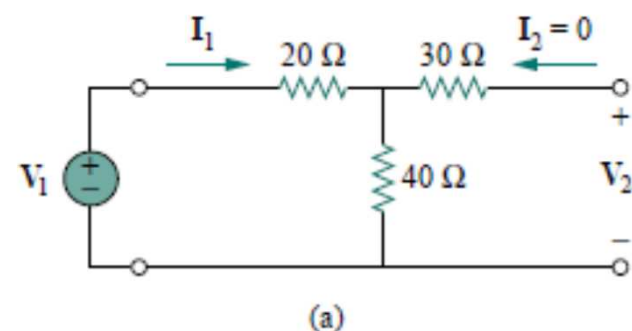

Method 2


Alternatively, since there is no dependent source in the given circuit, $z_{12} = z_{21}$ and we can use Fig. 5(a). Comparing with Fig. 5(a), we get

$$\begin{aligned} z_{12} &= 40 \, \Omega = z_{21} \\ z_{11} - z_{12} &= 20 \quad \Rightarrow \quad z_{11} = 20 + z_{12} = 60 \, \Omega \\ z_{22} - z_{12} &= 30 \quad \Rightarrow \quad z_{22} = 30 + z_{12} = 70 \, \Omega \end{aligned}$$

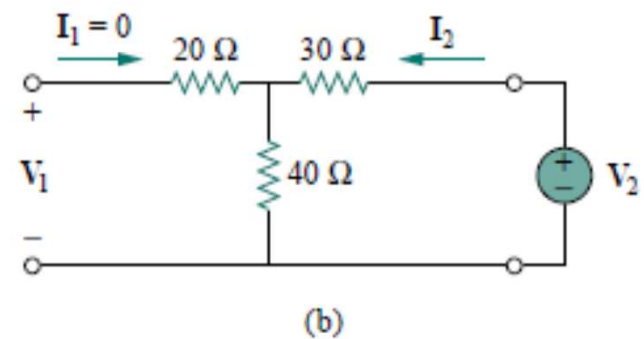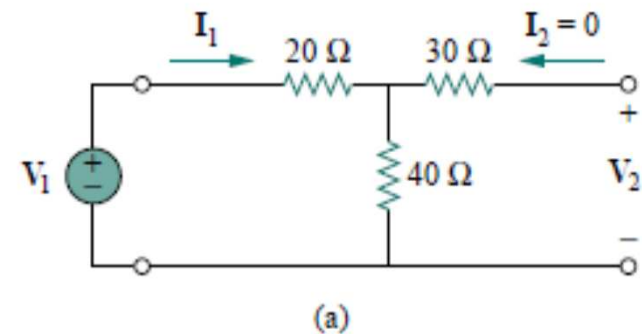

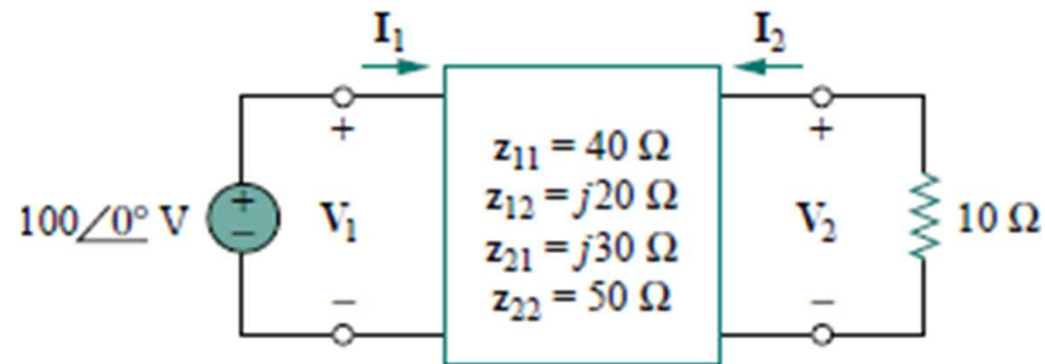Example 2

- Find I_1 and I_2 in the circuit of the following figure:



Example 2 Find I_1 and I_2 in the circuit in the following figure.

Solution:

we can use Eq. (1) directly. Substituting the given Z parameters into Eq. (1),

$$V_1 = 40I_1 + j20I_2$$

$$V_2 = j30I_1 + 50I_2$$

since we are looking for I_1 and I_2 , we substitute

$$V_1 = 100\angle 0^\circ, \quad V_2 = -10I_2$$

into the above Eqs., which become

$$100 = 40I_1 + j20I_2$$


$$-10I_2 = j30I_1 + 50I_2 \quad \Rightarrow \quad I_1 = j2I_2$$

Substituting we get

$$100 = j80I_2 + j20I_2 \quad \Rightarrow \quad I_2 = \frac{100}{j100} = -j$$

$$I_1 = j2(-j) = 2. \text{ Thus,}$$
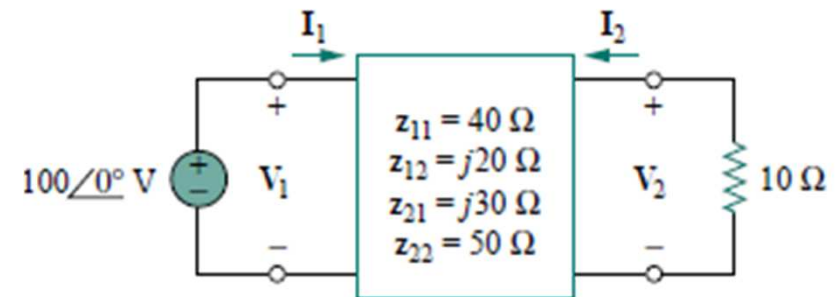
$$I_1 = 2\angle 0^\circ \text{ A}, \quad I_2 = 1\angle -90^\circ \text{ A}$$




ADMITTANCE PARAMETERS

- Impedance parameters may not exist for a two-port network. So there is a need for an alternative means of describing such a network. This need is met by the second set of parameters,
- In either Fig. 6(a) or (b), the terminal currents can be expressed in terms of the terminal voltages:
- The y terms are known as the *admittance parameters*
- (or, simply, *y parameters*)
- and have units of **siemens**.


$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

or in matrix form as
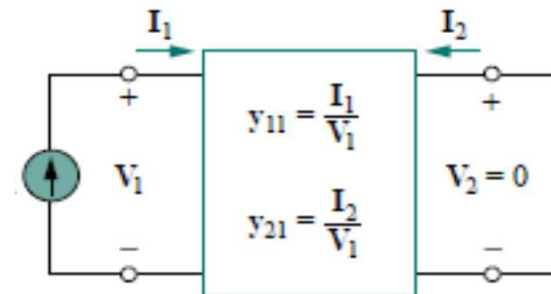
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



(a)

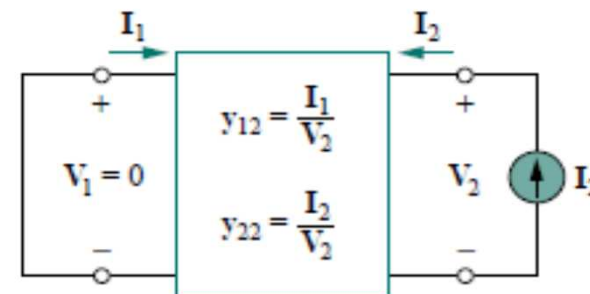


(b)




$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}, \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}, \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

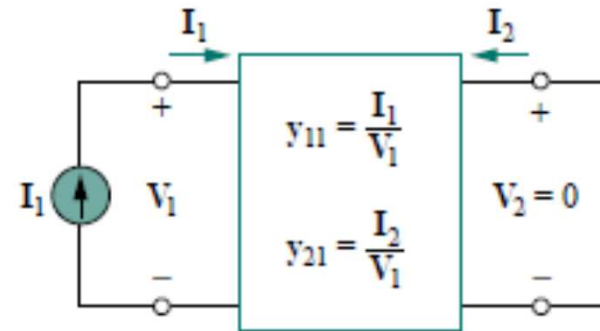

(a)

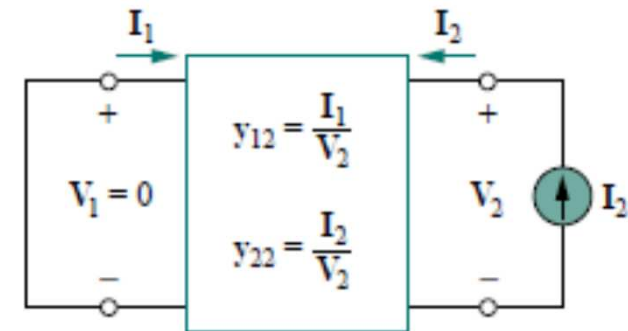


(b)

- Y_{11} = Short-circuit input admittance
 - Y_{12} = Short-circuit transfer admittance from port 2 to port 1
 - Y_{21} = Short-circuit transfer admittance from port 1 to port 2
 - Y_{22} = Short-circuit output admittance
- We obtain y_{11} and y_{21} by connecting a current I_1 to port 1 and short-circuiting port 2 as in Fig. 6(a), finding V_1 and I_2





When a two-port network has no dependent sources, the transfer admittances are equal ($y_{12} = y_{21}$).

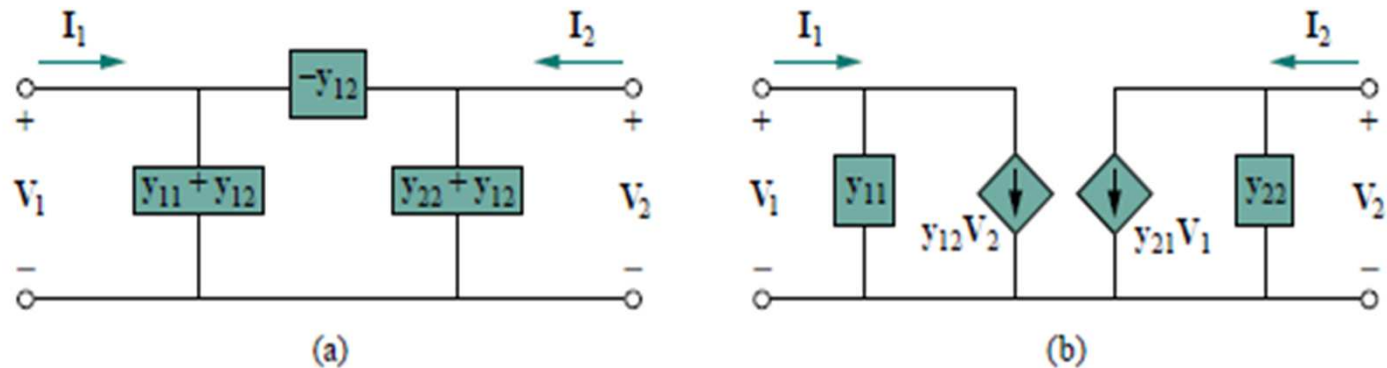- A reciprocal network ($y_{12} = y_{21}$) can be modeled by the π -equivalent circuit in Fig. 7(a).
- If the network is not reciprocal, a more general equivalent network is shown in Fig. 7(b).




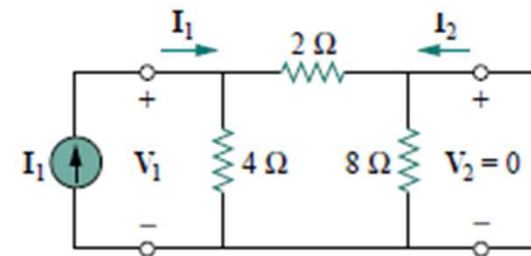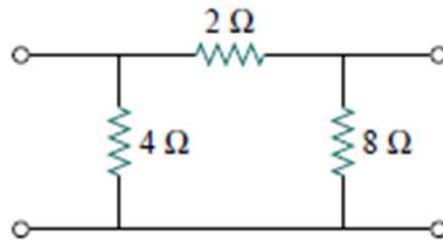Example .3

- Obtain the y parameters for the network shown in the following figure:



(a)

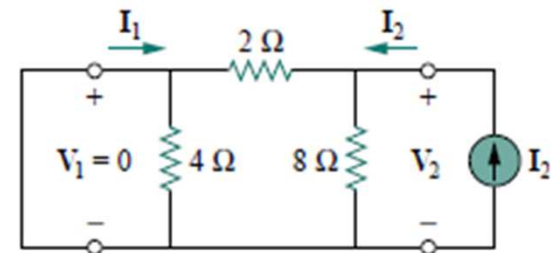

(b)



Solution:


- method1

To find y_{11} and y_{21} , short-circuit the output port and connect a current source I_1 to the input port as in Fig. (a). Since the $8\text{-}\Omega$ resistor is short-circuited, the $2\text{-}\Omega$ resistor is in parallel with the $4\text{-}\Omega$ resistor. Hence,

$$V_1 = I_1(4 \parallel 2) = \frac{4}{3}I_1, \quad y_{11} = \frac{I_1}{V_1} = \frac{I_1}{\frac{4}{3}I_1} = 0.75 \text{ S}$$

By current division,
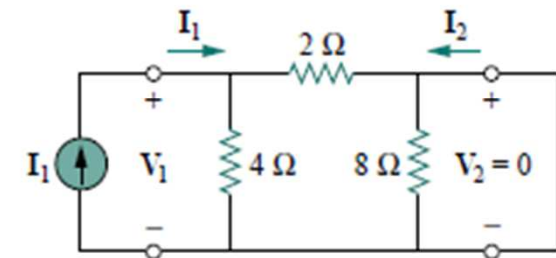
$$-I_2 = \frac{4}{4+2}I_1 = \frac{2}{3}I_1, \quad y_{21} = \frac{I_2}{V_1} = \frac{-\frac{2}{3}I_1}{\frac{4}{3}I_1} = -0.5 \text{ S}$$



(a)



Con.


- Method 1

To get y_{12} and y_{22} , short-circuit the input port and connect a current source I_2 to the output port as in Fig. (b). The 4- Ω resistor is short-circuited so that the 2- Ω and 8- Ω resistors are in parallel.

$$V_2 = I_2(8 \parallel 2) = \frac{8}{5}I_2, \quad y_{22} = \frac{I_2}{V_2} = \frac{I_2}{\frac{8}{5}I_2} = \frac{5}{8} = 0.625 \text{ S}$$

By current division,
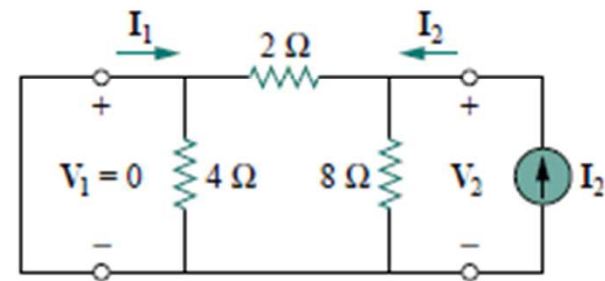
$$-I_1 = \frac{8}{8+2}I_2 = \frac{4}{5}I_2, \quad y_{12} = \frac{I_1}{V_2} = \frac{-\frac{4}{5}I_2}{\frac{8}{5}I_2} = -0.5 \text{ S}$$



(b)



Method 2



- Alternatively, comparing the original figure with Fig. (a),

$$y_{12} = -\frac{1}{2} \text{ S} = y_{21}$$


$$y_{11} + y_{12} = \frac{1}{4} \quad \Rightarrow \quad y_{11} = \frac{1}{4} - y_{12} = 0.75 \text{ S}$$

$$y_{22} + y_{12} = \frac{1}{8} \quad \Rightarrow \quad y_{22} = \frac{1}{8} - y_{12} = 0.625 \text{ S}$$

- As obtained previously

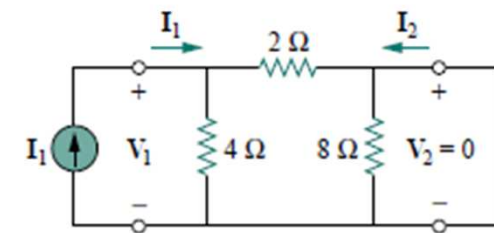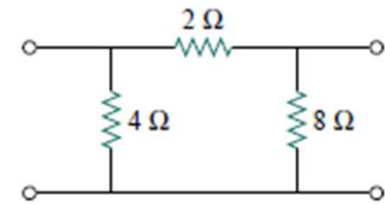

(a)

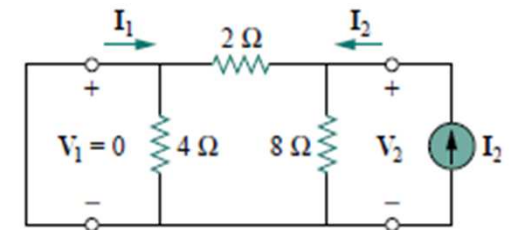

(b)



HYBRID PARAMETERS

- This third set of parameters is based on making V_1 and I_2 the dependent variables.

$$\begin{cases} V_1 = h_{11}I_1 + h_{12}V_2 \\ I_2 = h_{21}I_1 + h_{22}V_2 \end{cases}$$

or in matrix form,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

- The h terms are known as the *hybrid parameters* (or, *h parameters*)
- The ideal transformer can be described by the hybrid parameters.



The values of the parameters are determined as


$$\begin{aligned} h_{11} &= \left. \frac{V_1}{I_1} \right|_{V_2=0}, & h_{12} &= \left. \frac{V_1}{V_2} \right|_{I_1=0} \\ h_{21} &= \left. \frac{I_2}{I_1} \right|_{V_2=0}, & h_{22} &= \left. \frac{I_2}{V_2} \right|_{I_1=0} \end{aligned}$$

- h_{11} = Short-circuit input impedance
- h_{12} = Open-circuit reverse voltage gain
- h_{21} = Short-circuit forward current gain
- h_{22} = Open-circuit output admittance
- This is why they are called the hybrid parameters.



h parameters

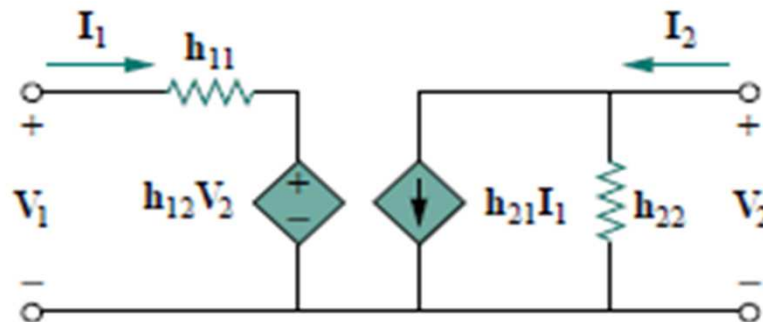- The procedure for calculating the h parameters is similar to that used for the z or y parameters.
- For reciprocal networks, $h_{12} = -h_{21}$. This can be proved in the same way as we proved that $z_{12} = z_{21}$.
- The following figure shows the hybrid model of a two-port network:



A set of parameters closely related to the h parameters are the g parameters or inverse hybrid parameters

- These are used to describe the terminal currents and voltages as:

$$\begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2 \\ V_2 &= g_{21}V_1 + g_{22}I_2 \end{aligned}$$


$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [g] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

- The values of the g parameters are determined as:

$$\begin{aligned} g_{11} &= \left. \frac{I_1}{V_1} \right|_{I_2=0}, & g_{12} &= \left. \frac{I_1}{I_2} \right|_{V_1=0} \\ g_{21} &= \left. \frac{V_2}{V_1} \right|_{I_2=0}, & g_{22} &= \left. \frac{V_2}{I_2} \right|_{V_1=0} \end{aligned}$$






- g_{11} = Open-circuit input admittance
- g_{12} = Short-circuit reverse current gain
- g_{21} = Open-circuit forward voltage gain
- g_{22} = Short-circuit output impedance
- The following figure shows the inverse hybrid model of a two-port network

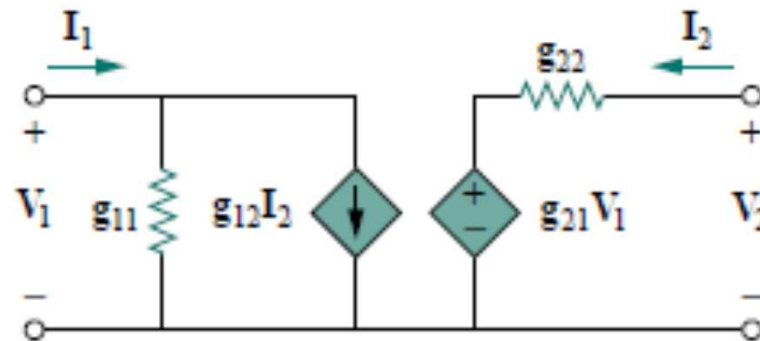

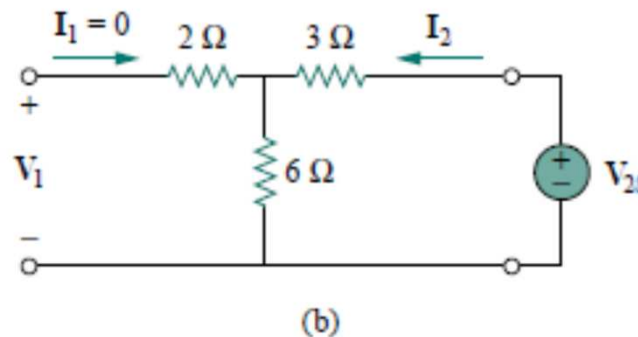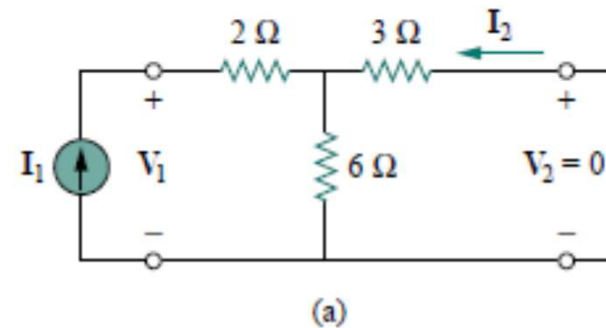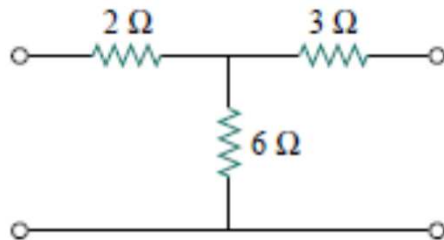Example 5

- Find the hybrid parameters for the two-port network of the following figure:



Example 5 Find the hybrid parameters for the two-port network of the following figure:

To find h_{11} and h_{21} , we short-circuit the output port and connect a current source I_1 to the input port as shown in Fig. (a). From Fig. (a),

$$V_1 = I_1(2 + 3 \parallel 6) = 4I_1$$

Hence,




$$h_{11} = \frac{V_1}{I_1} = 4 \Omega$$

Also, from Fig. (a) we obtain, by current division,

$$-I_2 = \frac{6}{6+3}I_1 = \frac{2}{3}I_1$$

Hence,
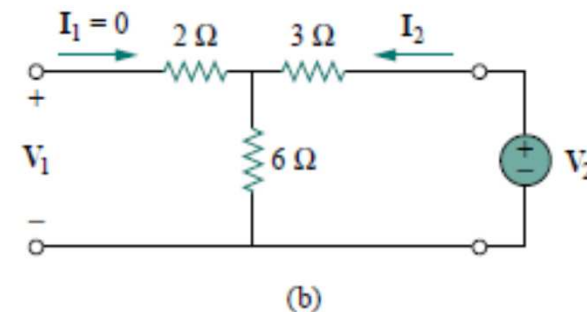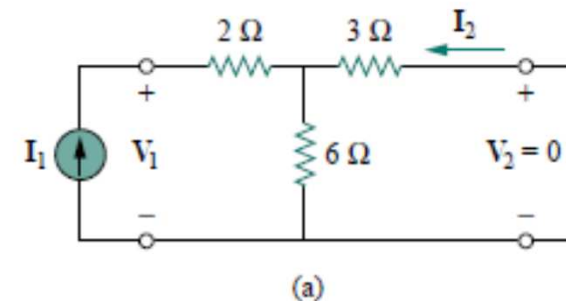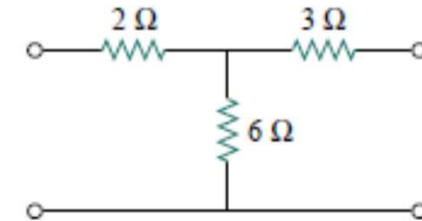
$$h_{21} = \frac{I_2}{I_1} = -\frac{2}{3}$$



Example 5 con.

To obtain h_{12} and h_{22} , we open-circuit the input port and connect a voltage source V_2 to the output port as in Fig. (b). By voltage division,

$$V_1 = \frac{6}{6+3} V_2 = \frac{2}{3} V_2$$

Hence,




$$h_{12} = \frac{V_1}{V_2} = \frac{2}{3}$$

Also,

$$V_2 = (3 + 6)I_2 = 9I_2$$

Thus,
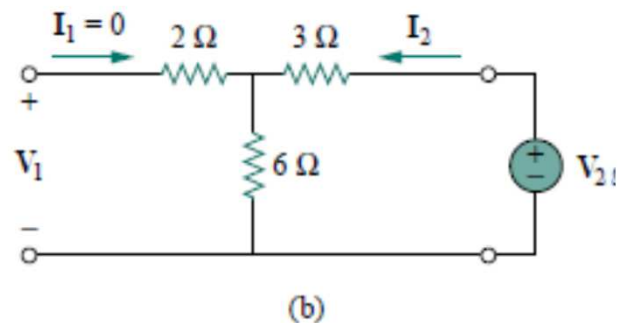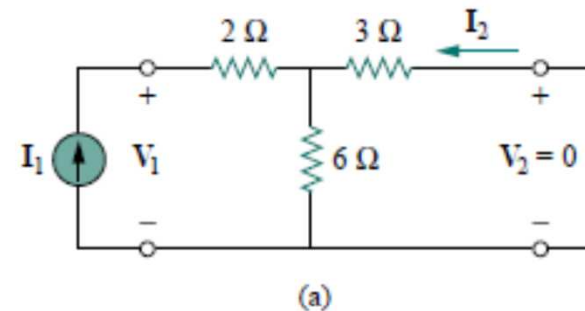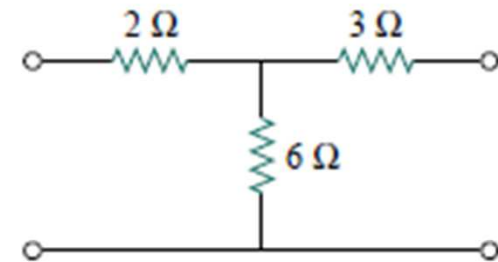
$$h_{22} = \frac{I_2}{V_2} = \frac{1}{9} \text{ S}$$



TRANSMISSION PARAMETERS

- The impedance and admittance parameters are grouped into the *immittance parameters*
- The term immittance denotes a quantity that is either an impedance or an admittance .
- The *a* parameters describe the voltage and current at one end of the two-port network in term of the voltage and current at the other end ,therefore they called the *transmission parameters*
- a_{11} = Open-circuit voltage ratio
- a_{12} =Negative short-circuit transfer impedance
- a_{22} =Open circuit transfer admittance
- a_{21} =Negative short-circuit current ratio

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$a_{12} = \left. -\frac{V_1}{I_2} \right|_{V_2=0} \Omega$$

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} \text{ S}$$

$$a_{22} = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$



b parameters

- The parameters *b* are called
- the *inverse* transmission parameters

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0}$$

$$b_{12} = - \left. \frac{V_2}{I_1} \right|_{V_1=0} \Omega$$

$$b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0} \text{ S}$$

$$b_{22} = - \left. \frac{I_2}{I_1} \right|_{V_1=0}$$

- b_{11} = Open-circuit voltage gain
- b_{12} = Negative short-circuit transfer impedance
- b_{22} = Open circuit transfer admittance
- b_{21} = Negative short-circuit current gain



RELATIONSHIPS BETWEEN PARAMETERS

- Since the six sets of parameters relate the same input and output terminal variables of the same two-port network, they should be interrelated.
- If two sets of parameters exist, we can relate one set to the other set.
- Given the z parameters, let us obtain the y parameters.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

or

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z]^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Also, we know that :

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Comparing Eqs we see that

$$[y] = [z]^{-1}$$



The adjoint of the $[z]$ matrix is

$$\begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}$$

and its determinant is

$$\Delta_z = z_{11}z_{22} - z_{12}z_{21}$$

Substituting these into Eq. $[y] = [z]^{-1}$, we get

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \frac{\begin{bmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{bmatrix}}{\Delta_z}$$

Equating terms yields

$$y_{11} = \frac{z_{22}}{\Delta_z}, \quad y_{12} = -\frac{z_{12}}{\Delta_z}, \quad y_{21} = -\frac{z_{21}}{\Delta_z}, \quad y_{22} = \frac{z_{11}}{\Delta_z}$$



As a second example, let us determine the h parameters from the z parameters. we know that,

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

Making I_2 the subject of second Eq.,

$$I_2 = -\frac{z_{21}}{z_{22}}I_1 + \frac{1}{z_{22}}V_2$$

Substituting this into first Eq.,

$$V_1 = \frac{z_{11}z_{22} - z_{12}z_{21}}{z_{22}}I_1 + \frac{z_{12}}{z_{22}}V_2$$

Putting Eqs in matrix form,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{\Delta_z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ -\frac{z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$



- For h parameters,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Comparing this with the last Eq., we obtain

$$h_{11} = \frac{\Delta_z}{z_{22}}, \quad h_{12} = \frac{z_{12}}{z_{22}}, \quad h_{21} = -\frac{z_{21}}{z_{22}}, \quad h_{22} = \frac{1}{z_{22}}$$

- It can also be shown that

$$[g] = [h]^{-1}$$

- Table 18.1 provides the conversion formulas for the six sets of two-port parameters. Given one set of parameters.



TABLE 18.1 Conversion of two-port parameters.

	z		y		h		g		T		t	
z	z_{11}	z_{12}	$\frac{y_{22}}{\Delta_y}$	$-\frac{y_{12}}{\Delta_y}$	$\frac{\Delta_h}{h_{22}}$	$\frac{h_{12}}{h_{22}}$	$\frac{1}{g_{11}}$	$-\frac{g_{12}}{g_{11}}$	$\frac{A}{C}$	$\frac{\Delta_T}{C}$	$\frac{d}{c}$	$\frac{1}{c}$
	z_{21}	z_{22}	$-\frac{y_{21}}{\Delta_y}$	$\frac{y_{11}}{\Delta_y}$	$-\frac{h_{21}}{h_{22}}$	$\frac{1}{h_{22}}$	$\frac{g_{21}}{g_{11}}$	$\frac{\Delta_g}{g_{11}}$	$\frac{1}{C}$	$\frac{D}{C}$	$\frac{\Delta_t}{c}$	$\frac{a}{c}$
y	$\frac{z_{22}}{\Delta_z}$	$-\frac{z_{12}}{\Delta_z}$	y_{11}	y_{12}	$\frac{1}{h_{11}}$	$-\frac{h_{12}}{h_{11}}$	$\frac{\Delta_g}{g_{22}}$	$\frac{g_{12}}{g_{22}}$	$\frac{D}{B}$	$-\frac{\Delta_T}{B}$	$\frac{a}{b}$	$-\frac{1}{b}$
	$-\frac{z_{21}}{\Delta_z}$	$\frac{z_{11}}{\Delta_z}$	y_{21}	y_{22}	$\frac{h_{21}}{h_{11}}$	$\frac{\Delta_h}{h_{11}}$	$-\frac{g_{21}}{g_{22}}$	$\frac{1}{g_{22}}$	$-\frac{1}{B}$	$\frac{A}{B}$	$-\frac{\Delta_t}{b}$	$\frac{d}{b}$
h	$\frac{\Delta_z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	h_{11}	h_{12}	$\frac{g_{22}}{\Delta_g}$	$-\frac{g_{12}}{\Delta_g}$	$\frac{B}{D}$	$\frac{\Delta_T}{D}$	$\frac{b}{a}$	$\frac{1}{a}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta_y}{y_{11}}$	h_{21}	h_{22}	$-\frac{g_{21}}{\Delta_g}$	$\frac{g_{11}}{\Delta_g}$	$-\frac{1}{D}$	$\frac{C}{D}$	$\frac{\Delta_t}{a}$	$\frac{c}{a}$
g	$\frac{1}{z_{11}}$	$-\frac{z_{12}}{z_{11}}$	$\frac{\Delta_y}{y_{22}}$	$\frac{y_{12}}{y_{22}}$	$\frac{h_{22}}{\Delta_h}$	$-\frac{h_{12}}{\Delta_h}$	g_{11}	g_{12}	$\frac{C}{A}$	$-\frac{\Delta_T}{A}$	$\frac{c}{d}$	$-\frac{1}{d}$
	$\frac{z_{21}}{z_{11}}$	$\frac{\Delta_z}{z_{11}}$	$-\frac{y_{21}}{y_{22}}$	$\frac{1}{y_{22}}$	$-\frac{h_{21}}{\Delta_h}$	$\frac{h_{11}}{\Delta_h}$	g_{21}	g_{22}	$\frac{1}{A}$	$\frac{B}{A}$	$\frac{\Delta_t}{d}$	$-\frac{b}{d}$
T	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta_z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	$-\frac{\Delta_h}{h_{21}}$	$\frac{h_{11}}{h_{21}}$	$\frac{1}{g_{21}}$	$\frac{g_{22}}{g_{21}}$	A	B	$\frac{d}{\Delta_t}$	$\frac{b}{\Delta_t}$
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta_y}{y_{21}}$	$\frac{y_{11}}{y_{21}}$	$-\frac{h_{22}}{h_{21}}$	$\frac{1}{h_{21}}$	$\frac{g_{11}}{g_{21}}$	$\frac{\Delta_g}{g_{21}}$	C	D	$\frac{c}{\Delta_t}$	$\frac{a}{\Delta_t}$
t	$\frac{z_{22}}{z_{12}}$	$\frac{\Delta_z}{z_{12}}$	$-\frac{y_{11}}{y_{12}}$	$-\frac{1}{y_{12}}$	$\frac{1}{h_{12}}$	$\frac{h_{11}}{h_{12}}$	$-\frac{\Delta_g}{g_{12}}$	$-\frac{g_{22}}{g_{12}}$	$\frac{D}{\Delta_T}$	$\frac{B}{\Delta_T}$	a	b
	$\frac{1}{z_{12}}$	$\frac{z_{11}}{z_{12}}$	$-\frac{\Delta_y}{y_{12}}$	$\frac{y_{22}}{y_{12}}$	$\frac{h_{22}}{h_{12}}$	$\frac{\Delta_h}{h_{12}}$	$-\frac{g_{11}}{g_{12}}$	$\frac{1}{g_{12}}$	$\frac{C}{\Delta_T}$	$\frac{A}{\Delta_T}$	c	d
$\Delta_z = z_{11}z_{22} - z_{12}z_{21}, \quad \Delta_h = h_{11}h_{22} - h_{12}h_{21}, \quad \Delta_T = AD - BC$ $\Delta_y = y_{11}y_{22} - y_{12}y_{21}, \quad \Delta_g = g_{11}g_{22} - g_{12}g_{21}, \quad \Delta_t = ad - bc$												



$$\begin{aligned} z_{11} &= \left. \frac{V_1}{I_1} \right|_{I_2=0}, & z_{12} &= \left. \frac{V_1}{I_2} \right|_{I_1=0} \\ z_{21} &= \left. \frac{V_2}{I_1} \right|_{I_2=0}, & z_{22} &= \left. \frac{V_2}{I_2} \right|_{I_1=0} \end{aligned}$$

$$\begin{aligned} y_{11} &= \left. \frac{I_1}{V_1} \right|_{V_2=0}, & y_{12} &= \left. \frac{I_1}{V_2} \right|_{V_1=0} \\ y_{21} &= \left. \frac{I_2}{V_1} \right|_{V_2=0}, & y_{22} &= \left. \frac{I_2}{V_2} \right|_{V_1=0} \end{aligned}$$

$$\begin{aligned} h_{11} &= \left. \frac{V_1}{I_1} \right|_{V_2=0}, & h_{12} &= \left. \frac{V_1}{V_2} \right|_{I_1=0} \\ h_{21} &= \left. \frac{I_2}{I_1} \right|_{V_2=0}, & h_{22} &= \left. \frac{I_2}{V_2} \right|_{I_1=0} \end{aligned}$$

$$\begin{aligned} g_{11} &= \left. \frac{I_1}{V_1} \right|_{I_2=0}, & g_{12} &= \left. \frac{I_1}{I_2} \right|_{V_1=0} \\ g_{21} &= \left. \frac{V_2}{V_1} \right|_{I_2=0}, & g_{22} &= \left. \frac{V_2}{I_2} \right|_{V_1=0} \end{aligned}$$

